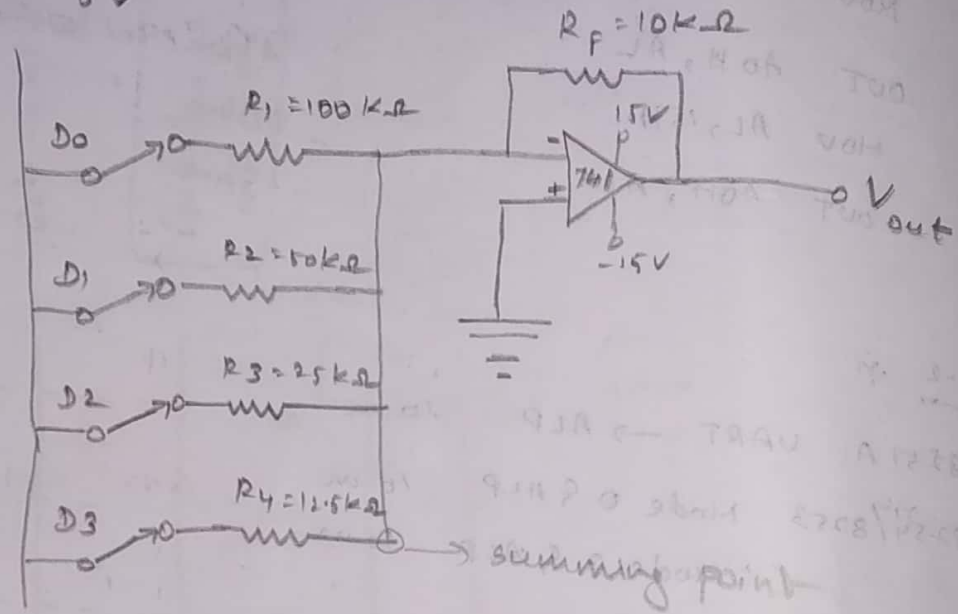


DIGITAL TO ANALOG CONVERTOR

purpose \rightarrow to convert a binary word to a proportional current (or) voltage

$$V_{ref} = -5V$$




D_0	D_1	D_2	D_3
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
1	1	1	1

weighted resistor \rightarrow

$$\begin{aligned} R_1 &= R \\ R_2 &= R/2 \\ R_3 &= R/4 \\ R_4 &= R/8 \end{aligned}$$

PARALLEL COMPARATOR A/D CONVERTER

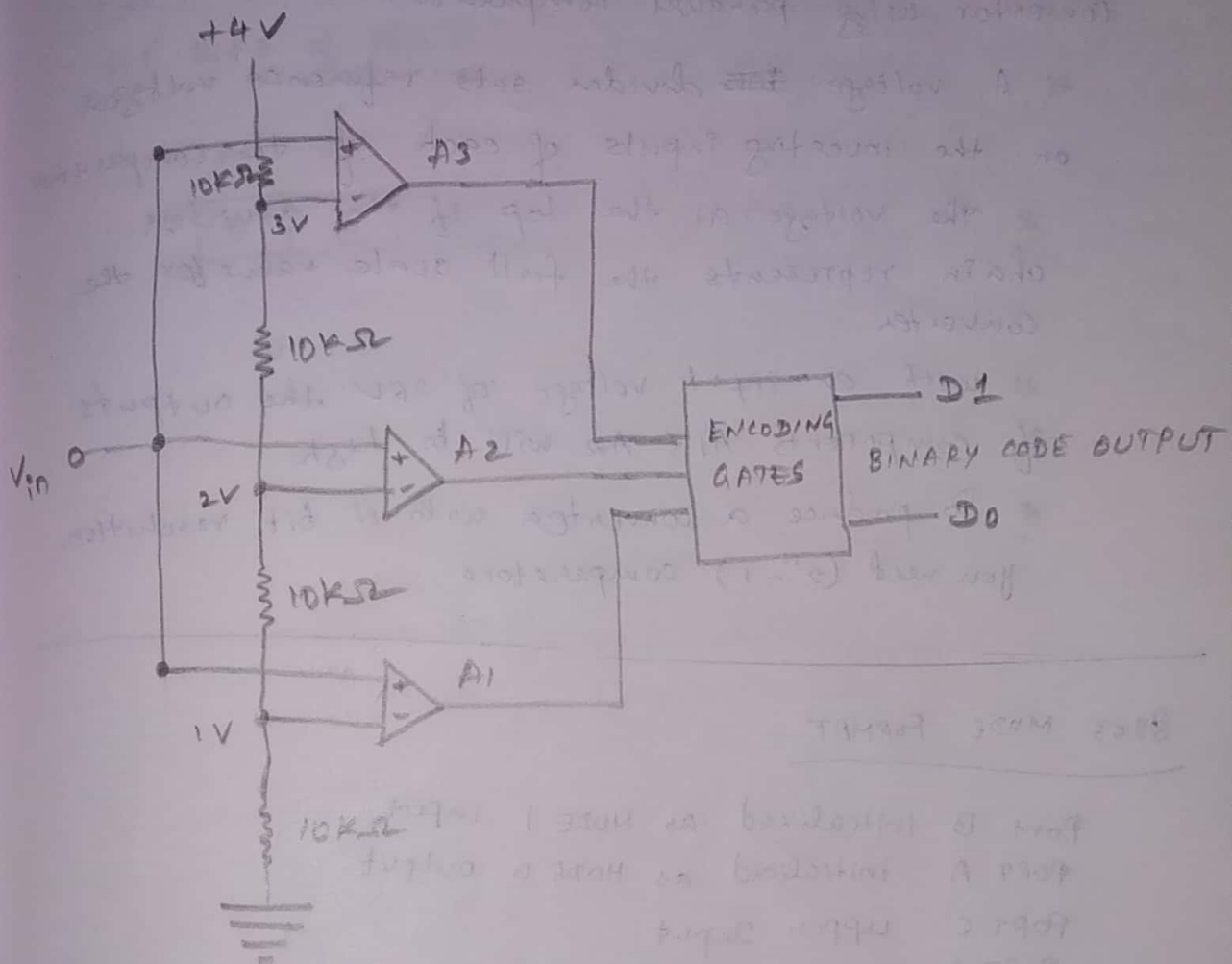

Suppose $V_{in} = 2.6$

$1V < 2.6 \rightarrow A_1 = \text{High}$
 $2V < 2.6 \rightarrow A_2 = \text{High}$
 $3V > 2.6 \rightarrow A_3 = \text{Low}$

10 bit digital signal $\Rightarrow (2^N - 1)$ converter

Advantage
faster

Disadv

↑ bits ↑ cost ↑ converter

* Shown is the circuit for 2-bit A/D converter using parallel comparators

* A voltage ~~in~~ divider sets reference voltages on the inverting inputs of each of the comparators

* the voltage at the top of the divider chain represents the full scale value for the converter

* with an input voltage of 2.6V the outputs of components A1 & A2 will be high

* To produce a converter with N bit resolution you need $(2^N - 1)$ comparators
